

**Question Paper Profile**

**Program Name** : Electrical Engineering Program Group  
**Program Code** : EE/EP/EU  
**Semester** : Third  
**Course Title** : Electrical Circuits  
**Max. Marks** : 70

22324

**Time: 3 Hrs.**

---

**Instructions:**

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

**Q.1 Attempt any Five of the following. 10 Marks**

- a) Draw impedance triangle for R-C series circuit. Write nature of power factor of this circuit.
- b) Define impedance and reactance related to single phase AC series circuit. Give the units of both.
- c) Define admittance with unit.
- d) Draw the sinusoidal waveform of 3-phase emf and also indicate the phase sequence.
- e) Give four steps to solve mesh analysis.
- f) State Superposition Theorem.
- g) State the maximum power transfer theorem for DC circuit.

**Q.2 Attempt any Three of the following. 12 Marks**

- a) Find active, reactive and apparent power and power factor of the A.C. Series circuit consisting of  $R=1 \text{ ohm}$ ,  $L=0.001 \text{ Henry}$  and  $C= 1 \text{ microfarad}$  supplied with 100 volt, 50 Hz power supply.
- b) A voltage of  $200 \angle 53^\circ$  is applied across two impedances in parallel. The values of impedances are  $(12 + j16)$  and  $(10 - j20)$ . Determine the kVA, kVAR and kW in each branch and power factor of the whole circuit.
- c) A delta connected induction motor is supplied by 3-phase, 400V, 50Hz supply the line current is 43.3A and the total power taken from the supply is 24 kW. Find the resistance and reactance per phase of motor winding
- d) Using mesh analysis find values of  $V_R$  as shown in Figure No. 1

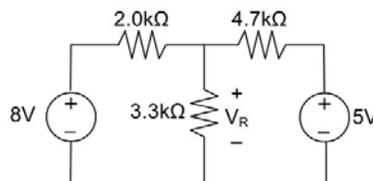


Fig. 1.

**Q.3) Attempt any Three of the following. 12 Marks**

- a) A coil of resistance  $50 \Omega$  and inductance of  $0.1 \text{ H}$  is connected in series with  $100 \text{ mF}$  capacitor. The combination is supplied with  $230 \text{ V}$ ,  $50 \text{ Hz}$  A.C. supply. Calculate voltage across each, current through the circuit, power factor and draw complete vector diagram.

- b) Two impedances  $(12 + j16)$  and  $(10 - j20) \Omega$  are connected in parallel across a supply of  $200 \angle 60^\circ$  using admittance method calculate branch currents, total current and power factor of whole circuit.
- c) Give four advantages of polyphase circuits over 1-phase circuits.
- d) Give the expression for star to delta and delta to star transformation.
- e) Using Norton's theorem, find current through  $1 \text{ohm}$  resistances in Figure No. 2.

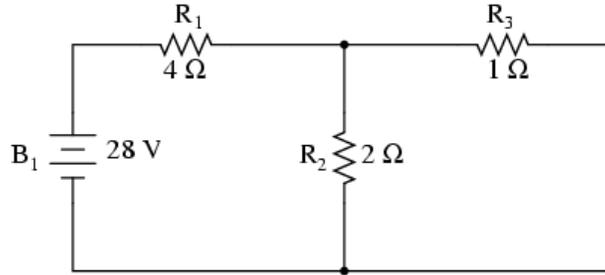


Fig.2

**Q.4) Attempt any Three of the following.**

**12 Marks**

- a) An inductive coil  $(10 + j40) \Omega$  impedance is connected in series with a capacitor of  $100 \mu\text{F}$  across  $230 \text{ V}$ ,  $50 \text{ Hz}$ , 1-Phase supply mains find :
  - (1) Current through the circuit
  - (2) P.F. of the circuit
  - (3) Power dissipated in the circuit
  - (4) Draw phasor diagram
- b) A coil having resistance of  $5 \Omega$  and inductance of  $0.2 \text{ H}$  is arranged in parallel with another coil having resistance of  $1 \Omega$  and inductance of  $0.08 \text{ H}$ . Calculate the current through the combination and power absorbed when a voltages of  $100 \text{ V}$ ,  $50 \text{ Hz}$  is applied. Use impedance method.
- c) Each phase of a delta-connected load comprises a resistor of  $50 \Omega$  and capacitor of  $50 \mu\text{F}$  in series. Calculate the line and phase currents when the load is connected to a  $440 \text{ V}$ , 3 phase  $50 \text{ Hz}$  supply.
- d) Define duality of electric circuits and write duality of electrical elements.

**Q.5) Attempt any Two of the following.**

**12 Marks**

- a) A  $100 \Omega$  resistor,  $0.02 \text{ H}$  inductor and  $1.2 \mu\text{F}$  capacitor are connected in parallel with a circuit made up of resistor of  $110 \Omega$  and a capacitor of  $2.4 \mu\text{F}$ . a supply of  $230 \text{ V}$ ,  $50 \text{ Hz}$  is connected across the circuit. Calculate the current taken from the supply & phase angle of it.
- b) Using source transformation, find the voltage across  $12 \Omega$  ( $v_x$ ), as shown in figure 3.

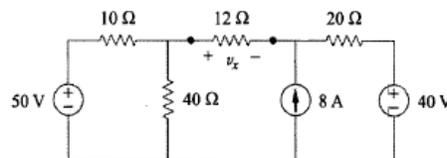


Fig.3

- c) Apply Thevenin's theorem to calculate current flowing through  $R_5 = 250 \Omega$  resistor as shown in figure.4

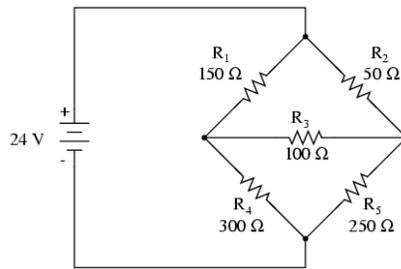


Fig.4

**Q.6) Attempt any Two of the following.**

**12 Marks**

- An a.c. series circuit has a resistance of 10  $\Omega$ , an inductance of 0.2 H and a capacitance of 60  $\mu\text{F}$ . Calculate: (a) resonant frequency (b) current (c) power at resonance. Applied voltage is 200 V.
- State relationship between line voltage and phase voltage, line current & phase current in a balanced star connection. Draw complete phasor diagram of voltages & current.
- Apply Superposition theorem to calculate current flowing through  $R_4 = 10 \Omega$  resistor as shown in figure.5

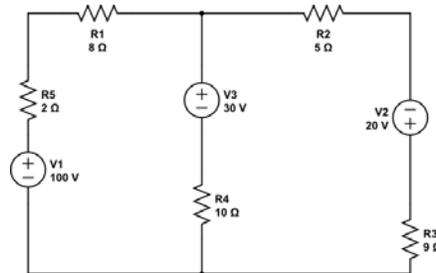


Fig.5

**'I' Scheme**

**Question Paper Profile**

**Program Name** : **Electrical Engineering Program Group**  
**Program Code** : **EE/EP/EU**  
**Semester** : **Third**  
**Course Title** : **Electrical Circuits**  
**Max. Marks** : **20**

22324

**Time: 1 Hour**

---

**Instructions:**

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

**Q.1 Attempt any FOUR.**

**08 Marks**

- a. Draw voltage triangles for R-L and R-C single phase AC series circuits.
- b. Define quality factor of series A.C. circuit.
- c. Convert  $Z = 6 + j8 \Omega$  in polar form.
- d. Define admittance and conductance in relation with parallel circuits. Give formulas for the same.
- e. Write properties of Parallel resonance.
- f. Define Quality Factor for parallel resonance. Give equation of it.

**Q.2 Attempt any THREE.**

**12 Marks**

- a. A resistance  $60 \Omega$  and inductance of  $0.5 \text{ H}$  is connected in series. The combination is supplied with  $230 \text{ V}$ ,  $50 \text{ Hz}$  A.C. supply. Calculate voltage across each, current through the circuit, power factor and draw complete vector diagram.
- b. A RC series circuit consisting of  $R = 10 \Omega$  and  $C = 100 \text{ mF}$  is connected across  $200\text{V}$ ,  $50\text{Hz}$  AC supply. Find the value of current and power factor. What will be the value of current and power factor if the value of resistance is doubled?
- c. Derive an expression for resonant frequency of a series RLC circuit.
- d. Impedances  $Z_1 = (10 + j5) \Omega$  and  $Z_2 = (8 + j6) \Omega$  are connected in parallel across  $V = (200 + j0)$ . Using the admittance method, calculate circuit current and the branch currents.
- e. A coil having resistance of  $5 \Omega$  and inductance of  $0.2\text{H}$  is arranged in parallel with capacitor of  $50 \mu\text{F}$ . Calculate the current through the combination and power absorbed when a voltages of  $100 \text{ V}$ ,  $50 \text{ Hz}$  is applied. Use impedance method.

Question Paper Profile

Program Name : Electrical Engineering Program Group  
Program Code : EE/EP/EU  
Semester : Third  
Course Title : Electrical Circuits  
Max. Marks : 70

22324

Time: 3 Hrs.

Instructions:

- (1) All questions are compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.
- (5) Preferably, write the answers in sequential order.

Q.1 Attempt any FOUR.


08 Marks

- a) Define line voltage and phase voltage
- b) What do you mean by balanced load and balanced supply in relation with polyphase AC circuits?
- c) Give four steps to solve nodal analysis.
- d) How current source can be converted into equivalent voltage source?
- e) State Reciprocity Theorem.
- f) State Norton's theorem.


Q.2 Attempt any THREE.

12 Marks

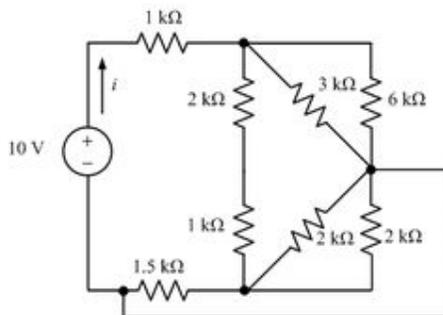- a. Three coils each with a resistance of  $10 \Omega$  and inductance of  $0.35\text{mH}$  are connected in star to a 3-phase,  $440 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate the line current and total power taken per phase.
- b. Derive relation between line and phase voltages of star connection of 3ph load.
- c. Find current in  $1\text{k} \Omega$  by using star delta transformation.



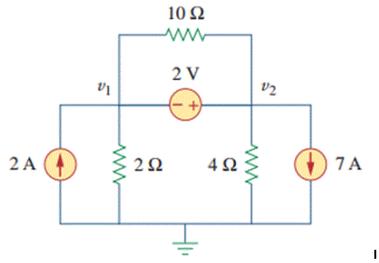- d. Find the current in  $10 \Omega$  by using superposition theorem.



e. Find maximum power in  $R_1 = 4 \Omega$  by using maximum power transfer theorem.

