

22421

21819

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

5 × 2 = 10

- (a) Construct OR gate using NAND gate.
- (b) Compare Harrod and Non-Neuman architecture. (any two points)
- (c) Write the excitation table for T-FF.
- (d) Define : (i) Address bus (ii) Data bus.
- (e) List the different addressing modes of 8051.
- (f) Define : (i) Assembler (ii) Compiler
- (g) Find the number of address lines required for
 - (i) 4K RAM (ii) 8K ROM

2. Attempt any THREE of the following :

3 × 4 = 12

- (a) State & explain De-Morgan's first theorem.
- (b) Compare microprocessor & microcontroller. (any four points)
- (c) Solve the following SOP expressions with the help of K-map :
 - (i) $F(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 7)$
 - (ii) $F(A, B, C) = \sum m(0, 1, 4, 5, 6, 7)$
- (d) Write any two laws of Boolean algebra. Justify with the help of truth table.

3. Attempt any THREE of the following :**12**

- (a) List any eight features of microcontroller 8051.
- (b) Compare TTL, CMOS & ECL families on the following :
 - (i) Power dissipation
 - (ii) Noise Margin
 - (iii) Speed of Operation
 - (iv) Fan-in
- (c) Describe the function of following pins of 8051 :
 - (i) $\overline{\text{PSEN}}$
 - (ii) RESET
 - (iii) ALE
 - (iv) $\overline{\text{EA}}$
- (d) Draw logic diagram of 4 : 1 multiplexer & give it's truth table.

4. Attempt any THREE of the following :**12**

- (a) Draw a neat labelled interfacing diagram of 8051 with stepper motor.
- (b) Implement OR gate using transistor.
- (c) Write the alternative function of Port-3 pins.
- (d) Draw master-slave JK FF & write it's truth table.
- (e) Explain Boolean processor of 8051.

5. Attempt any TWO of the following :**12**

- (a) Execute the following program & specify the contents of Accumulator & status of PSW after execution. Also draw the format of PSW
 - MoV A, #0FH
 - MoV B, #03H
 - Div AB
 - End
- (b) Develop an ALP to generate square wave of 1kHz at port pin P1.3. Draw flowchart for it.
- (c) Explain full adder with it's logic diagram & truth table.

6. Attempt any TWO of the following :**12**

- (a) Construct 3-bit synchronous UP counter using flipflop. Also draw it's timing diagram.
 - (b) Describe the following assembler directives with one example of each :
 - (i) ORG
 - (ii) DB
 - (iii) EQU
 - (iv) END
 - (v) CODE
 - (vi) DATA
 - (c) Develop an ALP for interfacing of LED's with Port 1 of 8051. Draw interfacing diagram for the same.
-

